

EE405(B), Fall 2022

Electronics Design Lab. <Advanced Digital System Design>

- Student Names: Hyemin Lee
- Student IDs: 20190533
- LAB Project Number: Lab0, Lab1

1. Goal / Specification

A. Lab 0

- i. The goal of this lab project is to setup the FPGA development environment. The development environment will be constructed using FPGA design tools (Xilinx Vivado & Xilinx Vitis) and FPGA evaluation board (Xilinx Arty A7-35T).
- ii. Field Programmable Gate Array (FPGA) is VLSI circuit that consists of programmable logic blocks, IO blocks, and interconnections. A board named Xilinx Arty A7-35T will be used for all the projects in this course.
- iii. Vivado is hardware design tool for synthesis and implementation on Xilinx's FPGAs. It also supports simulation and analysis of HDL designs.
- iv. Vitis is software design tool for creating embedded software applications on Xilinx's microprocessors. It also supports C/C++ based design, debug, and performance analysis.

B. Lab 1

- i. The goal of this lab project is to learn whole process of FPGA programming with a simple example of LED display.
- ii. The first problem (Problem 1A) was to implement an LED blinking system using buttons (BTN0 and BTN1) and LED (LD4). The BTN0 was reset button and the BTN1 was enabling button for LD4.
- iii. The second problem (Problem 1B) was to implement an LED counter system using buttons (BTN0, 1, 2) and RGB LEDs (LD0, 1, 2, 3). The BTN0 was reset button. The BTN1 was used to increase the number of the counter, and BTN2 was used to change the RGB LEDs color among red, green, and blue.

2. Architecture / Design


A. Description

- i. Problem 1A: Implement an LED blinking system
 1. Input ports: `i_clk` (clock), `i_rst` (BTN0), `i_en` (BTN1)
 2. Output ports: `o_led` (LD4)
 3. A single flip-flop named `led` was used and directly assigned to `o_led`.


4. If i_rst is 1, led becomes 0, and if i_en is 1, led becomes 1. Nothing happens when i_st or i_en is 0.
- ii. Problem 1B: Implement an LED counter system
1. Input ports: i_clk (clock), i_rst (BTN0), i_en (BTN1), i_ch_color (BTN2)
 2. Output ports: $o_led_red[3:0]$, $o_led_green[3:0]$, $o_led_blue[3:0]$
 3. MSB 0 of each output port was connected to red, green, and blue of LD0. MSB 1 of each output port was connected to red, green, and blue of LD1. In the same manner, MSB 2 and MSB 3 were connected to LD2 and LD3.
 4. Five flip-flops named n , $color$, led_red , led_green , and led_blue were used. led_red , led_green , and led_blue were directly assigned to o_led_red , o_led_green , and o_led_blue , respectively.
 5. All the flip-flops were updated to the next value synchronously at positive edge of every clock. The next value was calculated through combinational logic in between clocks.
 6. Nothing happened if i_en or i_ch_color is 0.
 7. If i_en is 1, the value of n increased by 1. But reset to 0 if the value exceeds 15, the maximum number counter can calculate.
 8. If i_ch_color is 1, the value of $color$ increased by 1. But reset to 0 if the value exceeds 2. This was because there are only three colors: red(0), green(1), and blue(2).
 9. According to the value of n and $color$, led_red , led_green , and led_blue was updated. If $color$ was 0, led_red updated to n while led_green and led_blue became 0. If $color$ was 1, led_green updated to n while led_red and led_blue became 0. Lastly, if $color$ was 2, led_blue updated to n while led_red and led_green became 0.

B. Hardware Block Diagram (Use Visio, at least Power point, etc., **Don't draw by hand**)

i. Problem 1A

 

ii. Problem 1B


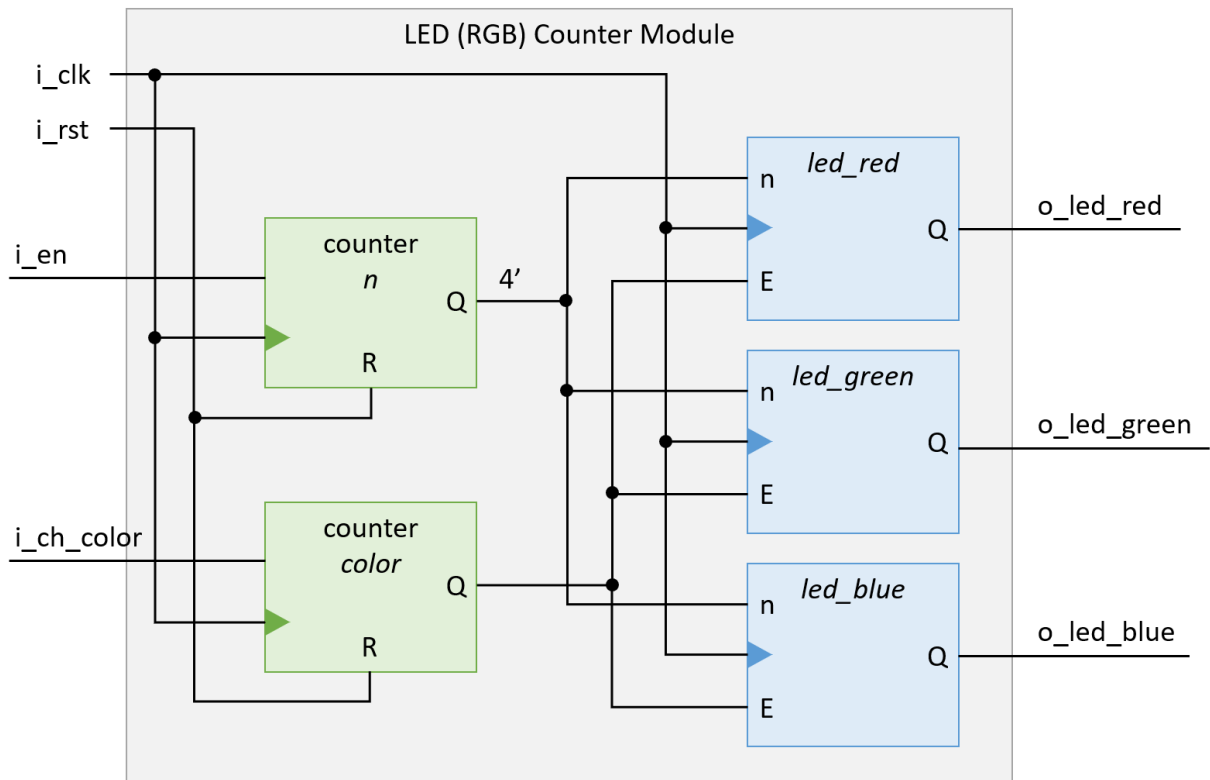


3. Experiment Results

A. Demo Picture


i. Problem 1A

  1. (Left) Press BT1: Turn on LD4
2. (Right) Press BT0: Turn off LD4



ii. Problem 1B

 
1. Press BT1: Increase the counter number from 0000_2 to 1111_2 .



2. Press BT2: Change color in order of red, green, and blue.



3. Press BT0: Reset the counter.

 

4. Discussion

A. Explain briefly about the Vivado IP and Microblaze.

- i. IP stands for Intellectual Property. Xilinx provides numerous libraries of pre-validated IP cores to help users get to market faster. In Vivado, there is IP integrator that allows users to easily interconnect complex IP blocks.
- ii. MicroBlaze is Xilinx's 32-bit RISC soft processor core, optimized for embedded applications on Xilinx devices. It is implemented entirely in the general-purpose memory and logic fabric of Xilinx FPGAs which meets the requirements of many diverse applications including Industrial, Medical, Automotive, Consumer, and Communications markets. It includes three preset configurations – Microcontroller, Real-Time Processor, and Application Processor – to help users quickly deploy their application.

B. In Lab0, we synthesized the Microblaze to the Arty A7 board. Explain why we did it and how we can utilize the Microblaze.

- i. We do synthesis to convert the schematic design to FPGA-specific LUTs and other primitive components. It creates Xilinx specific netlist files that are required during implementation process.

- ii. Using Microblaze, we can accelerate the development of const-sensitive, high-volume applications that traditionally required one or more microcontrollers. Especially, since Arty A7 board is one of the Xilinx's Cost-Optimized Portfolio FPGAs, it offers advances in tool suite and FPGA platform to help simplify development effort and minimize system budgets. Microblaze can be utilized in various fields such as industrial, communications infrastructure, medical device, automotive, and consumer markets.
- C. Explain the difference between Verilog and SystemVerilog (in terms of usage, syntax, etc.).
- i. The main difference between Verilog and SystemVerilog is that Verilog is a Hardware Description Language (HDL), while SystemVerilog is a HDL and Hardware Verification Language (HVL) based on Verilog. HDL is used to model electronic systems, and HVL is used to verify the electronic circuits written in a HDL. Overall, SystemVerilog is a superset of Verilog.
 - ii. Verilog only supports structured paradigm, while SystemVerilog supports structured and object-oriented paradigms. Also, Verilog only supports wire and reg data types, while SystemVerilog supports various data types such as enum, struct, union, class and string in addition to wire and reg.
 - iii. The file extension of Verilog is .v or .vh, while that of SystemVerilog is .sv or .svh. Verilog has a single always block to implement combinational and sequential logic, while SystemVerilog has always_comb, always_ff, and always_latch procedural blocks to implement.
- D. Explain briefly about the FPGA implementation process.
- i. Implementation is the process of determining which physical resources on the FPGA to program with which logic, and how to connect (route) them. This produces the bitstream that is loaded onto the device for FPGA programming.
- E. In the LED counter system, there might be a problem that the counter increases several times even if the button is pressed once. Why does this problem occur, and how did you solve this problem?
- i. Since uncountable number of clock passes while pressing the button, if you only write the code like 'if (i_en == 1) n = n + 1', the counting number will increase countlessly. Therefore, I proposed a new variable named *pressing_i_en* and *pressing_i_ch_color*. These variables act as flag and indicates whether the button is holding. If the button is released, the flag resets its value and wait for another pressing.
 - ii. However, although I introduced *pressing_i_en* and *pressing_i_ch_color*, the counter often increased several times as mentioned in the question. This was due to vibration of switch. In order to solve this problem, switch debouncing technique should be implemented. The technique saves the old value of the switch and maintains the value for certain period of times so that the

flickering of input does not directly reflected as result. I'll implement this technique from the next project.

5. Appendix: Include your code here

A. Problem 1A

```
module LED(  
    // input ports  
    input wire    i_clk    ,  
    input wire    i_rst    ,  
    input wire    i_en     ,  
    output wire    o_led  
);  
  
    // RTL Code  
    reg led;  
    initial led = 0;  
  
    // assign register to wire  
    assign o_led = led;  
  
    // sequential logic : operate with clock  
    always @ (posedge i_clk) begin  
        // Reset  
        if (i_rst) begin  
            led <= 0;  
        end  
        // Run  
        else begin  
            if (i_en) begin  
                led <= 1;  
            end  
        end  
    end  
end  
endmodule
```

B. Problem 1B

```

module LED(
    // input ports
    input wire    i_clk   ,
    input wire    i_rst   ,
    input wire    i_en    ,
    input wire    i_ch_color,
    output wire    [3:0] o_led_red,
    output wire    [3:0] o_led_green,
    output wire    [3:0] o_led_blue
);

    // RTL Code
    reg [3:0] n, nxt_n;
    reg [3:0] led_red, led_green, led_blue;
    reg [3:0] nxt_led_red, nxt_led_green, nxt_led_blue;
    reg [1:0] color, nxt_color;    // 0:red, 1:green, 2:blue
    reg pressing_i_en, pressing_i_ch_color;

    // assign register to wire
    assign o_led_red = led_red;
    assign o_led_green = led_green;
    assign o_led_blue = led_blue;

    // sequential logic : operate with clock
    always_ff @ (posedge i_clk) begin
        // Update LED
        n <= nxt_n;
        color <= nxt_color;
        led_red <= nxt_led_red;
        led_green <= nxt_led_green;
        led_blue <= nxt_led_blue;
    end

    // combinational logic
    always_comb begin
        if (i_rst) begin

```

```

    nxt_n = 0;
    nxt_led_red = 0;
    nxt_led_green = 0;
    nxt_led_blue = 0;
    nxt_color = 0;
end else begin
    // i_en: increase number
    if (i_en) begin                // button is pressed
        if (~pressing_i_en) begin // if this is the first clock while button
is pressed, increase the number
            if (n == 4'b1111) nxt_n = 0;
            else nxt_n = n + 1;
            pressing_i_en = 1;
        end
    end else begin                // if the button is released, reset
'pressing_i_en'
        if (pressing_i_en) pressing_i_en = 0;
    end

    // i_ch_color: change color
    if (i_ch_color) begin
        if (~pressing_i_ch_color) begin
            if (color == 2'b10) nxt_color = 0;
            else nxt_color = color + 1;
            pressing_i_ch_color = 1;
        end
    end else begin
        if (pressing_i_ch_color) pressing_i_ch_color = 0;
    end

    // Update the next LED color
    case (color)
        2'b00: begin                // red
            nxt_led_red = n;
            nxt_led_green = 0;
            nxt_led_blue = 0;
        end
        2'b01: begin                // green

```



```
        nxt_led_red = 0;
        nxt_led_green = n;
        nxt_led_blue = 0;
    end
    2'b10: begin          // blue
        nxt_led_red = 0;
        nxt_led_green = 0;
        nxt_led_blue = n;
    end
endcase
end
end
endmodule
```